

中国科学院大学计算机组成原理实验课

实 验 报 告

学号: 2015K8009929045 姓名: 张远航 专业: 计算机科学与技术

实验序号: 3 实验名称: 多周期处理器设计

注 1: 本实验报告请以 PDF 格式提交。文件命名规则: [学号]-PRJ[实验序号]-RPT.pdf, 其中文件名字母大写, 后缀名小写。例如: [2014K8009959088]-PRJ[1]-RPT.pdf
注 2: 实验报告模板以下部分的内容供参考, 可包含但不限定如下条目内容。

- 一、 逻辑电路结构与仿真波形的截图及说明 (比如关键 RTL 代码段 {包含注释} 及其对应的逻辑电路结构、相应信号的仿真波形和信号变化的说明等)
- 数据通路模块代码如下, 实现遵照 Patterson 在 COD 中给出的结构, 为了实现 LUI、SLL 等新操作加宽了 ALUSrc、RegDst 等信号。电路结构参见图 1。

```
1 module datapath(  
2     ... (port definition, omitted)  
3 );  
4  
5     // additional registers  
6     reg  [31:0] MDR, IR, ALUOut, A, B;  
7  
8     wire [4:0] rs, rt, rd, sa;  
9     wire [15:0] immediate;  
10  
11     reg  [31:0] nPC;  
12  
13     wire [31:0] sext_imm;  
14  
15     initial begin  
16         nPC = 32'b0;  
17     end  
18  
19     assign Op = IR[31:26];  
20     assign rs = IR[25:21];  
21     assign rt = IR[20:16];
```

```

22     assign rd = IR[15:11];
23     assign sa = IR[10:6];
24
25     assign immediate = IR[15:0];
26     assign sext_imm = {{(16){IR[15]}}}, immediate};
27     // we assign the Op field to func for I-type instructions
28     assign func = (ALUOp == 2'b11) ? IR[31:26]: IR[5:0];
29
30     // program counter
31     always @(*)
32         case (PCSource)
33             2'b00: nPC <= Result;
34             2'b01: nPC <= ALUOut;
35             2'b10: nPC <= {mips_PC[31:28], IR[25:0], 2'b00};
36             default: nPC <= Result;
37         endcase
38
39     // ALU
40     always @(*)
41         case (ALUSrcA)
42             2'b00: OpA = mips_PC;
43             2'b01: OpA = A;
44             2'b10: OpA = sa;
45             2'b11: OpA = 32'd16;
46         endcase
47
48     always @(*)
49         case (ALUSrcB)
50             2'b00: OpB = B;
51             2'b01: OpB = 32'd4;
52             2'b10: OpB = sext_imm;
53             2'b11: OpB = sext_imm << 2;
54         endcase
55
56     // register file
57     always @(*)
58         case (RegDst)
59             2'b00: waddr = rt;
60             2'b01: waddr = rd;

```

```

61         2'b10: waddr = 5'd31;    // JAL
62         default: waddr = 5'd0;
63     endcase
64
65     assign raddr1 = rs;
66     assign raddr2 = rt;
67     assign wen = RegWrite;
68     always @(*)
69         case (MemtoReg)
70             2'b00: wdata = ALUOut;
71             2'b01: wdata = MDR;
72             2'b10: wdata = Result;
73             default: wdata = Result;
74         endcase
75
76     // MIPS
77     assign mips_MemWrite = MemWrite;
78     assign mips_MemRead = MemRead;
79     assign mips_Address = ALUOut;
80     assign mips_Write_data = B;
81
82     always @(posedge clk) begin
83         if (rst) begin
84             IR <= 32'b0; MDR <= 32'b0;
85             mips_PC <= 32'b0;
86             A <= 32'b0; B <= 32'b0;
87             ALUOut <= 32'b0;
88         end
89         else begin
90             if (PCwen) mips_PC <= nPC;
91             if (IRWrite) IR <= mips_Instruction;
92             MDR <= mips_Read_data;
93             A <= rdata1;
94             B <= rdata2;
95             ALUOut <= Result;
96         end
97     end
98
99 endmodule

```

采用多级译码的 ALU 的控制单元，结构见图 2（为了区分不同的 SPECIAL 和 I 型指令，输入需增加 func 信号）：

```
1 module alu_control(  
2     input  [5:0] func,  
3  
4     input  [1:0] ALUOp,  
5     output reg [2:0] ALUctr  
6 );  
7  
8     ... (func code parameters, omitted)  
9     always @(*) begin  
10         case (ALUOp)  
11             2'b00: ALUctr <= OP_ADD;    // LW or SW  
12             2'b01: ALUctr <= OP_SUB;    // BEQ or BNE  
13             2'b10:                          // R-type  
14                 case (func)  
15                     SLL:  ALUctr <= OP_SLL;  
16                     ADDU: ALUctr <= OP_ADD;  
17                     OR:   ALUctr <= OP_OR;  
18                     // [$zero]+GPR[rs] = GPR[rs]  
19                     JR:   ALUctr <= OP_ADD;  
20                     SLT:  ALUctr <= OP_SLT;  
21                     default: ALUctr <= OP_NOP;  
22                 endcase  
23             2'b11:                          // I-type or J-type  
24                 case (func)  
25                     ADDIU: ALUctr <= OP_ADD;  
26                     SLTI:  ALUctr <= OP_SLT;  
27                     SLTIU: ALUctr <= OP_SLTU;  
28                     LUI:   ALUctr <= OP_LUI;  
29                     JAL:   ALUctr <= OP_ADD;  
30                     default: ALUctr <= OP_NOP;  
31                 endcase  
32             endcase  
33         end  
34  
35 endmodule
```

以及 CPU 的控制单元（多周期加入了 FSM）：

```

1  module control(
2      input  clk, rst, Zero,
3
4      input  [5:0] Op, func,
5      output reg [1:0] ALUOp, ALUSrcB, ALUSrcA, PCSource, RegDst,
        MentoReg,
6
7      output reg PCWriteCond, PCWrite, MemRead, MemWrite, IRWrite,
        RegWrite,
8      output wire PCwen
9  );
10
11      ... (opcode definition, omitted)
12      // FSM data selector
13      parameter FETCH = 4'b0000;           // instruction fetch
14      parameter DECODE = 4'b0001;         // instruction decode /
        register fetch
15      parameter MEMADDRCOMP = 4'b0010;     // memory address
        computation
16      parameter MEMACCESS_L = 4'b0011;    // memory access (LW)
17      parameter MEMRDEND = 4'b0100;       // memory read
        completion step
18      parameter MEMACCESS_S = 4'b0101;    // memory access (SW)
19      parameter RTYPEEXEC = 4'b0110;      // R-type execution
20      parameter RTYPEEND = 4'b0111;       // R-type completion
21      parameter BRANCHEND = 4'b1000;      // branch completion
22      parameter JMPEND = 4'b1001;         // jump completion
23      parameter ITYPEEXEC = 4'b1010;      // I-type execution
24      parameter ITYPEEND = 4'b1011;       // I-type completion
25      parameter JALEXEC = 4'b1100;        // JAL execution, step 1
26      parameter JREXEC = 4'b1101;        // JR execution
27      parameter SLLEXEC = 4'b1110;
28      parameter LUIEXEC = 4'b1111;
29
30      reg [3:0] state, nextstate;
31
32      // BNE or BEQ
33      assign PCwen = PCWrite | (PCWriteCond & (Op[0] ? !Zero :
        Zero));

```

```

34
35     // synchronous reset
36     always @(posedge clk)
37         if (rst)
38             state <= FETCH;
39         else
40             state <= nextstate;
41
42     // next state logic
43     always @(state or Op or func) begin
44         case (state)
45             FETCH: nextstate <= DECODE;
46             DECODE: case (Op)
47                 SPECIAL:
48                     case (func)
49                         JR: nextstate <= JREXEC;
50                         SLL: nextstate <= SLLEXEC;
51                         default: nextstate <= RTYPEEXEC;
52                     endcase
53             ADDIU, SLTI, SLTIU: nextstate <= ITYPEEXEC;
54             LUI: nextstate <= LUIEXEC;
55             BEQ, BNE: nextstate <= BRANCHEND;
56             J: nextstate <= JMPEND;
57             JAL: nextstate <= JALEXEC;
58             LW: nextstate <= MEMADDRCOMP;
59             SW: nextstate <= MEMADDRCOMP;
60             default: nextstate <= FETCH;
61         endcase
62         MEMADDRCOMP: case (Op)
63             LW: nextstate <= MEMACCESS_L;
64             SW: nextstate <= MEMACCESS_S;
65             default: nextstate <= FETCH;
66         endcase
67         JALEXEC: nextstate <= JMPEND;    // jump after PC+4
68         JREXEC: nextstate <= FETCH;
69         LUIEXEC: nextstate <= ITYPEEND;
70         SLLEXEC: nextstate <= RTYPEEND;
71         MEMACCESS_L: nextstate <= MEMRDEND;
72         RTYPEEXEC: nextstate <= RTYPEEND;

```

```

73         IYPEEEXEC: nextstate <= IYPEEEND;
74         MEMACCESS_S, MEMRDEND, IYPEEEND, RTYPEEND, BRANCHEND
           , JMPEND: nextstate <= FETCH;
75         default: nextstate <= FETCH;
76     endcase
77 end
78
79 always @(state) begin
80     case (state)
81         FETCH: {PCWriteCond, PCWrite, MemRead, MemWrite,
                 MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
                 ALUSrcB, RegWrite, RegDst} <= 18'
                 b0110_00_1_00_00_00_01_0_00;
82         DECODE: {PCWriteCond, PCWrite, MemRead, MemWrite,
                  MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
                  ALUSrcB, RegWrite, RegDst} <= 18'
                  b0000_00_0_00_00_00_11_0_00;
83         MEMADDRCOMP: {PCWriteCond, PCWrite, MemRead,
                       MemWrite, MemtoReg, IRWrite, PCSrc, ALUOp,
                       ALUSrcA, ALUSrcB, RegWrite, RegDst} <= 18'
                       b0000_00_0_00_00_01_10_0_00;
84         MEMACCESS_L: {PCWriteCond, PCWrite, MemRead,
                       MemWrite, MemtoReg, IRWrite, PCSrc, ALUOp,
                       ALUSrcA, ALUSrcB, RegWrite, RegDst} <= 18'
                       b0010_00_0_00_00_00_00_0_00;
85         MEMACCESS_S: {PCWriteCond, PCWrite, MemRead,
                       MemWrite, MemtoReg, IRWrite, PCSrc, ALUOp,
                       ALUSrcA, ALUSrcB, RegWrite, RegDst} <= 18'
                       b0001_00_0_00_00_00_00_0_00;
86         RTYPEEEXEC: {PCWriteCond, PCWrite, MemRead, MemWrite,
                      MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
                      ALUSrcB, RegWrite, RegDst} <= 18'
                      b0000_00_0_00_10_01_00_0_00;
87         RTYPEEEND: {PCWriteCond, PCWrite, MemRead, MemWrite,
                    MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
                    ALUSrcB, RegWrite, RegDst} <= 18'
                    b0000_00_0_00_00_00_00_1_01;
88         JREXEC: {PCWriteCond, PCWrite, MemRead, MemWrite,
                  MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,

```

```

        ALUSrcB, RegWrite, RegDst} <= 18'
        b0100_00_0_00_10_01_00_0_00;
89      SLLEXEC:  {PCWriteCond, PCWrite, MemRead, MemWrite,
        MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
        ALUSrcB, RegWrite, RegDst} <= 18'
        b0000_00_0_00_10_10_00_0_00;
90      LUIEXEC:  {PCWriteCond, PCWrite, MemRead, MemWrite,
        MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
        ALUSrcB, RegWrite, RegDst} <= 18'
        b0000_00_0_00_11_11_10_0_00;
91      // for the time being we use PC+4 for JAL
92      JALEXEC:  {PCWriteCond, PCWrite, MemRead, MemWrite,
        MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
        ALUSrcB, RegWrite, RegDst} <= 18'
        b0000_10_0_00_11_00_01_1_10;
93      ITYPEEXEC: {PCWriteCond, PCWrite, MemRead, MemWrite,
        MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
        ALUSrcB, RegWrite, RegDst} <= 18'
        b0000_00_0_00_11_01_10_0_00;
94      ITYPEEND:  {PCWriteCond, PCWrite, MemRead, MemWrite,
        MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
        ALUSrcB, RegWrite, RegDst} <= 18'
        b0000_00_0_00_00_00_00_1_00;
95      BRANCHEND: {PCWriteCond, PCWrite, MemRead, MemWrite,
        MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
        ALUSrcB, RegWrite, RegDst} <= 18'
        b1000_00_0_01_01_01_00_0_00;
96      MEMRDEND:  {PCWriteCond, PCWrite, MemRead, MemWrite,
        MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
        ALUSrcB, RegWrite, RegDst} <= 18'
        b0000_01_0_00_00_00_00_1_00;
97      JMPEND:    {PCWriteCond, PCWrite, MemRead, MemWrite,
        MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
        ALUSrcB, RegWrite, RegDst} <= 18'
        b0100_00_0_10_00_00_00_0_00;
98      default:  {PCWriteCond, PCWrite, MemRead, MemWrite,
        MemtoReg, IRWrite, PCSrc, ALUOp, ALUSrcA,
        ALUSrcB, RegWrite, RegDst} <= 18'b0;
99      endcase

```




```

100         end
101
102     endmodule


```

结构见图 3。


下面是一些仿真波形：

 

memcpy 程序执行结果

 

上板用程序执行结果，执行结束标志变量变为 0（以 bubble-sort 为例）

 

状态机状态信号的变化情况

二、 实验过程中遇到的问题、对问题的思考过程及解决方法（比如 RTL 代码中出现的逻辑 bug，仿真及上板调试过程中的难点等）

Bug 合集

- (a) 数据通路里，有信号在实例化的时候忘记接线了。
- (b) 译码器又有写错的……
- (c) 部分信号没有放进 `always` 块的敏感性列表里导致出错。

三、对讲义中思考题的理解和回答


无思考题

四、对于此次实验的心得、感受和建议（比如实验是否过于简单或复杂，是否缺少了某些你认为重要的信息或参考资料，以及其他想与任课老师交流的内容等）


- 有了前两次实验的基础，这次实验终于开始感觉比较轻松了，所以没有太多想说的……
- 原来 `.vh` 文件是可以直接包含进去的 ==
- 写译码器的时候中间插入下划线作为分隔符给了我很大的视觉辅助。
- 被助教哥哥的大规模测试用例吸引住了，自己也想搞一个了！

插图

1	数据通路	12
2	ALU 控制单元	13
3	控制单元	14

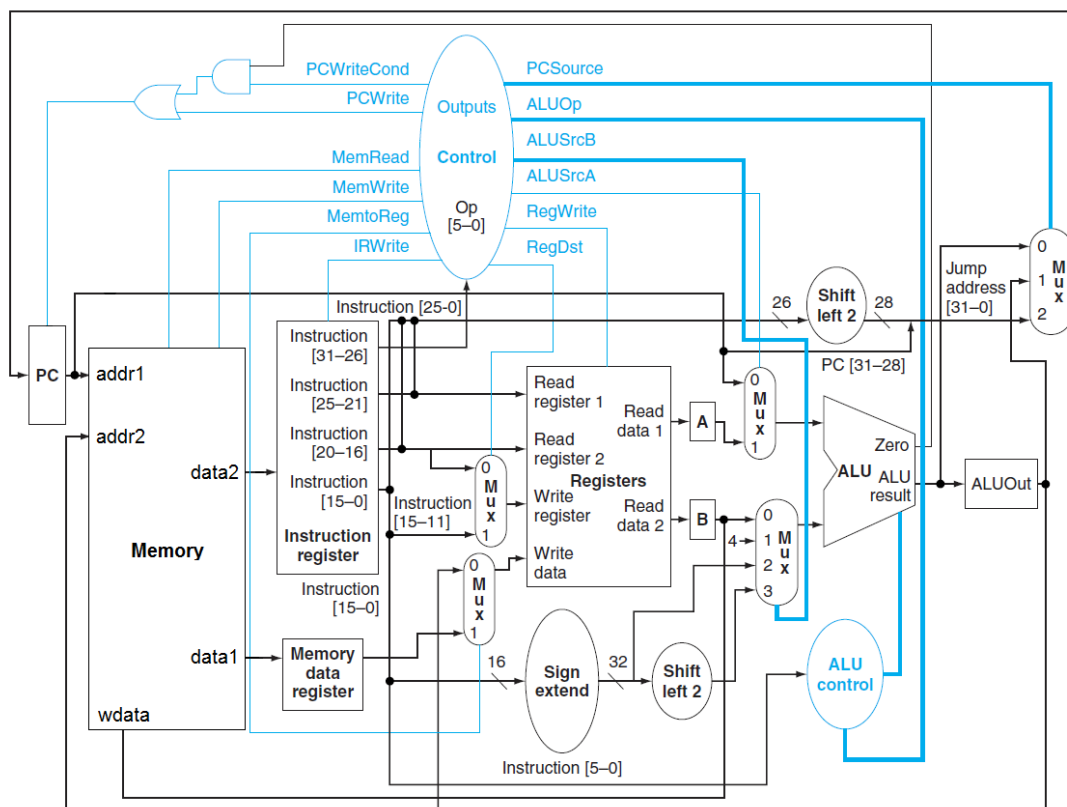

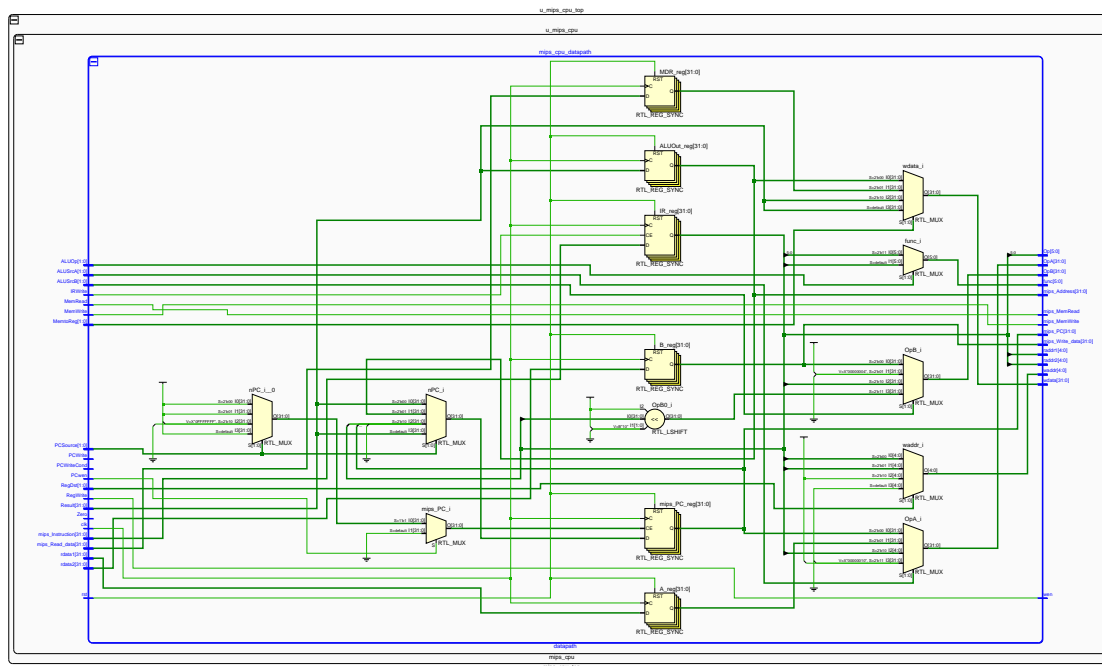(a) 期望的数据通路 (来源: Patterson & Hennessey, 2005, 有改动)



(b) 实现的 RTL 图

图 1: 数据通路

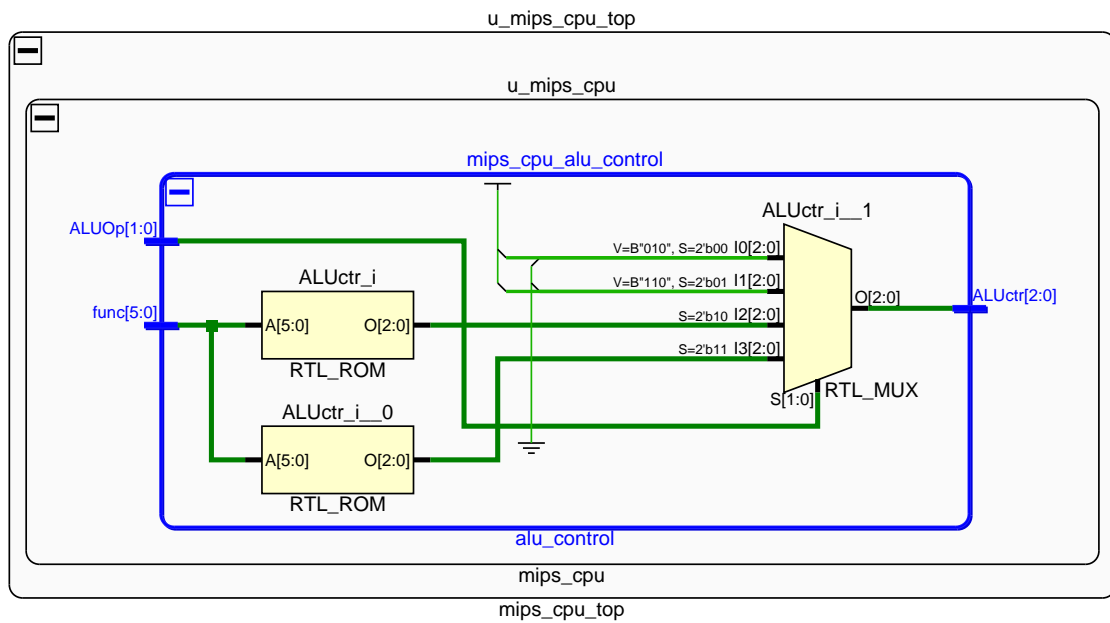


图 2: ALU 控制单元

